



C09-EC-305

**3237**

**BOARD DIPLOMA EXAMINATION, (C-09)  
MARCH/APRIL—2018  
DECE—THIRD SEMESTER EXAMINATION**

DIGITAL ELECTRONICS

Time : 3 hours ]

[ Total Marks : 80

**PART—A**

3×10=30

**Instructions** : (1) Answer **all** questions.

(2) Each question carries **three** marks.

(3) Answers should be brief and straight to the point and shall not exceed *five* simple sentences.

1. Define de Morgan's theorems with example.

2. Perform the following conversions :

(a)  $(CB4.C8)_{16}$  to decimal number system

(b)  $(1101100101)_2$  to its gray code equivalent

3. Realise the basic gates using NAND gates only.

4. Distinguish between serial adder and parallel adder.

5. What is the need for tri-state buffer? Give its symbolic representation.

6. Explain the need of preset and clear inputs in flip-flops.

\*

/3237

\*

1

[ Contd...

7. What is race <sup>\*</sup> around condition? How can it be avoided?
8. List any two IC numbers of flip-flops, registers and counters.
9. Classify various types of memories.
10. Define the terms :
  - (a) Resolution
  - (b) Monotonicity
  - (c) Settling time

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.  
(2) Each question carries **ten** marks.  
(3) Answers should be comprehensive and the criterion for valuation is the content but not the length of the answer.

11. (a) Draw and explain TTL NAND gate with totem-pole output. 7  
(b) Explain the importance of parity bit. 3
12. (a) Compare TTL, ECL and CMOS logic families. 6  
(b) What are min terms and max terms? Explain their significance. 4
13. Draw and explain a 4-bit parallel adder using full adders with suitable example.
14. (a) Draw and explain the operation of 1×4 demultiplexer. 6  
(b) Construct a full adder using NAND gates only. 4
15. Draw the logic and timing diagram of *J-K* master-slave flip-flop and explain its working.

- 16.** Draw and explain the working 74194 universal shift register and its importance. 6
- 17.** Explain analog to digital conversion using successive approximation method with a neat diagram. 4
- 18.** (a) What is NVRAM? Draw the block diagram of NVRAM. Explain its operation. 6
- (b) List the applications of digital to analog converters. 4

\*\*\*

302 302 302 302

http://www.sbtetonline.com