

STATE BOARD OF TECHNICAL EDUCATION AND TRAINING
TELANGANA
DIPLOMA EXAMINATION (C-21)
C21-MID1-AUG-2022
SEMESTER III , MID-I EXAM



EE-305
Electrical Circuits

PCODE
13028

Duration: 1 Hour

[Total Marks: 20]

526

PART-A

526

Instructions:

1. Answer the following questions.
2. Each question carries **ONE** mark.

4 X 1 = 4

1. Define Electric Network.
2. Define "Star circuit" configuration of resistances.
3. List the two Energy Sources
4. State Norton's theorem.

526

PART-B

526

Instructions:

1. Answer the following questions.
2. Each question carries **THREE** marks.

2 X 3 = 6

- 5(a). Three resistances 20Ω , 90Ω and 10Ω are connected in Star. Find the equivalent Delta

---- OR ----

- 5(b). State Kirchoff's laws.

- 6(a). Calculate the value of load resistance R_L to which maximum power may be transferred from the circuit shown in figure. Determine also the value of maximum power


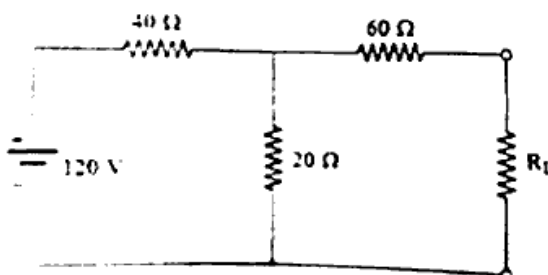


FIGURE :

---- OR ----

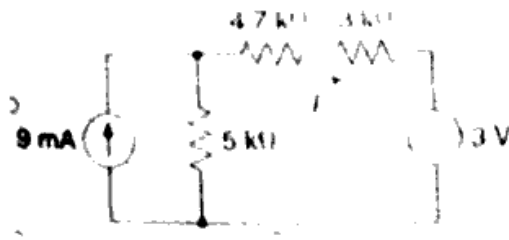
- 6(b). Compute the current through the $4.7\text{ k}\Omega$ resistor in figure using source transformation ?



PART-C


- Instructions:**
1. Answer the following questions. 2 X 5 = 10
 2. Each question carries **FIVE** marks.

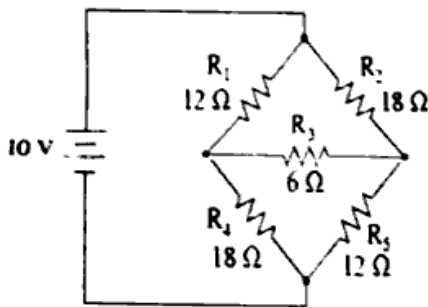- 7(a). Find the resistance between the terminals of the battery in bridge network as shown in Fig.1




----- OR -----

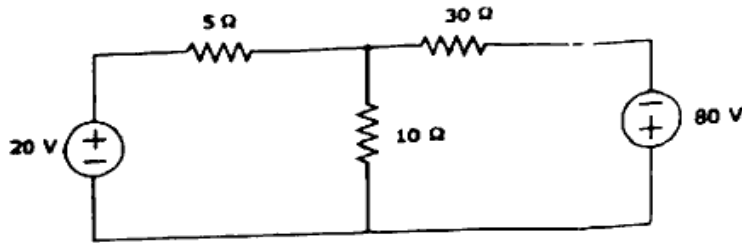- 7(b). Find the voltage across $30\ \Omega$ resistor using **Mesh analysis**.



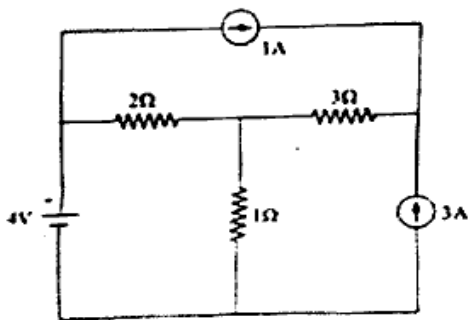- 8(a). In the circuit shown in fig . Find the current through 1Ω resistor using superposition theorem.



---- OR ----

- 8(b). State and Explain Thevenin's Theorem

<https://www.sbtetonline.com>
 Whatsapp @ 9300930012
 Send your old paper & get 10/-
 अपने पुराने पेपर्स भेजे और 10 रुपये पायें,
 Paytm or Google Pay से